

Embedded Electronics Lab

Ragesh Ramachandran
Vivekanandan Pazhanirajan

Question 1: To display number 5 on digit 0 of the 7-segment display of the Xilinx cool runner board.

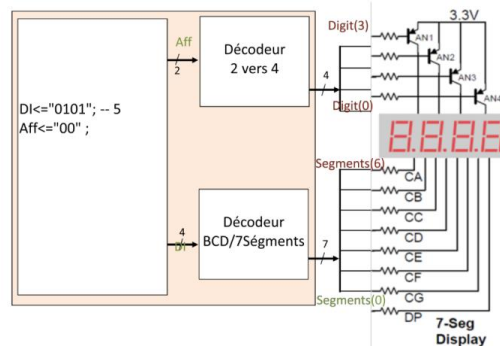


Fig 1: Circuit for the program 1

The program was done using the concept of components so we used three entity and their architecture. The first entity was for decoder which is necessary for selecting the corresponding digit on the seven-segment display. There are 4 digits in the display and each of these can be individually selected. Only 2-bits are necessary for the selection of 4 digits. So, the entity 'decoder' has input 'aff' which is a 'standard_logic_vector' of 2 bits and an output digit which is also a 'standard_logic_vector' of 4 bits. The architecture part of the decoder decides the behavior of the decoder. The 'aff' is used to select a particular 'digit' in the display

```
1
2 •library IEEE;
3   use IEEE.STD_LOGIC_1164.ALL;
4   use ieee.std_logic_arith.all;
5   use ieee.std_logic_unsigned.all;
6
7
8   entity decoder is port
9       (aff: in std_logic_vector (1 downto 0) ;
10        digit: out std_logic_vector (3 downto 0));
11   end decoder;
12
13   architecture archi_decoder of decoder is
14
15   begin
16       with aff select
17           digit <= "1110" when "00",
18                   "1101" when "01",
19                   "1011" when "10",
20                   "0111" when "11",
21                   "1111" when others;
22
23   end archi_decoder;
24
```

This part of the program is used to display digits in the seven-segment display using the 4-bit inputs. The seven-segment display can display 10 digit from 0 to 9.

The entity 'bcdTo7seg' part has 'di' as the input which is a 'std_logic_vector' of 4 bits and segments as the output which is a 'std_logic_vector' of 7 bits. The architecture 'arCbcdToseg' part decides the numbers (0 to 9) based on the input 'di'

```
25  library IEEE;
26  use IEEE.STD_LOGIC_1164.ALL;
27  use ieee.std_logic_arith.all;
28  use ieee.std_logic_unsigned.all;
29
30  entity bcdTo7seg is port
31  (di: in std_logic_vector (3 downto 0) ;
32   segments: out std_logic_vector (6 downto 0));
33  end bcdTo7seg;
34
35  architecture arCbcdTo7seg of bcdTo7seg is
36
37  begin
38      with di select
39          segments <= "0000001" when "0000",
40                      "1001111" when "0001",
41                      "0010010" when "0010",
42                      "0000110" when "0011",
43                      "1001100" when "0100",
44                      "0100100" when "0101",
45                      "0100000" when "0110",
46                      "0001111" when "0111",
47                      "0000000" when "1000",
48                      "0000100" when "1001",
49                      "1111111" when others;
50
51  end arCbcdTo7seg;
52
```

The entity 'program1' part has 'digit' as the output with 'std_logic_vector' of 4-bits' and 'segments' as the output with 'std_logic_vector' of 7-bits. The architecture 'Behavioural' part gets the signal 'aff' and 'di'. Now we use the decoder and 7-segment display written before as components in this program so we can reuse it. The components 'decoder' and 'bcdTo7seg' are defined in the architecture 'Behavioural' part. Now we use a command named "portmap" and using this 'aff' and 'digit' are port mapped and also the 'di' and 'segments' are port mapped. Now the output of the display is 5 on the digit at unit's place

```

50
51   end arCbcdTo7seg;
52
53   entity program1 is port
54       ( digit: out std_logic_vector (3 downto 0);
55         segments: out std_logic_vector (6 downto 0));
56   end program4;
57
58   architecture Behavioral of program1 is
59
60       signal aff: std_logic_vector (1 downto 0) ;
61       signal di: std_logic_vector (3 downto 0) ;
62
63       component decoder port
64           (aff: in std_logic_vector (1 downto 0) ;
65            digit: out std_logic_vector (3 downto 0));
66       end component;
67
68       component bcdTo7seg port
69           (di: in std_logic_vector (3 downto 0) ;
70            segments: out std_logic_vector (6 downto 0));
71       end component;
72
73   begin
74       aff = "00";
75       di = "0101"
76       digit: decoder port map ( aff,digit);
77       segment: bcdTo7seg port map (di,segments);
78
79   end Behavioral;
80

```

Question 2: To display value 0 on digit 0 of the Xilinx cool runner board.

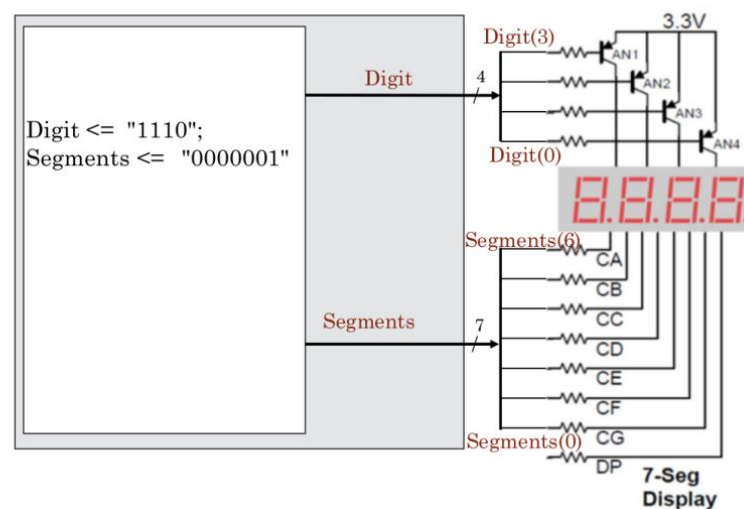


Fig 2: Circuit for the program 2

The same program was used for this question with only a small modification in the architecture 'Behavioral' part. This is the advantage of using the components it helps in using the code again with minor changes. So, in this program the 'aff' is assigned "00" which select the digit in unit's place and the digit is assigned "0000" which display the number '0' in the 7-segment display.

```
50
51   end arCbcdTo7seg;
52
53   entity program1 is port
54       ( digit: out std_logic_vector (3 downto 0);
55         segments: out std_logic_vector (6 downto 0));
56   end program4;
57
58   architecture Behavioral of program1 is
59
60       signal aff: std_logic_vector (1 downto 0) ;
61       signal di: std_logic_vector (3 downto 0) ;
62
63       component decoder port
64           (aff: in std_logic_vector (1 downto 0) ;
65            digit: out std_logic_vector (3 downto 0));
66       end component;
67
68       component bcdTo7seg port
69           (di: in std_logic_vector (3 downto 0) ;
70            segments: out std_logic_vector (6 downto 0));
71       end component;
72
73   begin
74       aff = "00";
75       di = "0000"
76       digit: decoder port map ( aff,digit);
77       segment: bcdTo7seg port map (di,segments);
78
79   end Behavioral;
80
```

Question 3: perform a scan of the display using counter to display the number 2018

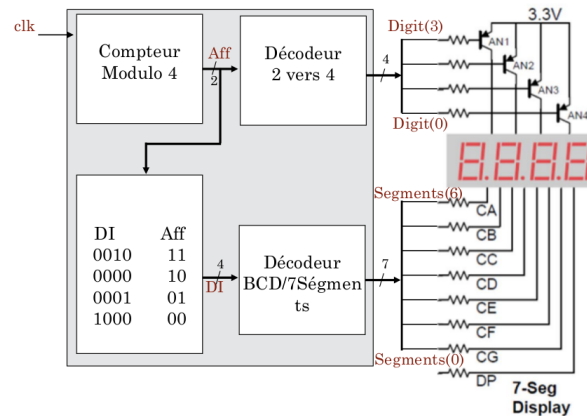


Fig 3: Circuit for the program 3

This program was done using 4 entities and they are:

- 'Decoder' for selecting the digit place to be displayed.
- 'BcdTo7seg' to display the digit in the 7-segment display.
- 'Counter' to do a modulo 4 counter and also uses this to display "2008" in the display.
- 'Prog4' to combine all these entity as components and display the output "2018"

The entity decoder has 'aff' as input of type 'std_logic_vector' of 2-bits and 'digit' as output of type 'std_logic_vector' of 4-bits. The architecture part of the decoder decides the behavior of the decoder. The 'aff' is used to select a particular 'digit' in the display.

```

2  library IEEE;
3  use IEEE.STD_LOGIC_1164.ALL;
4  use ieee.std_logic_arith.all;
5  use ieee.std_logic_unsigned.all;
6  -----
7  entity decoder is port
8      (aff: in std_logic_vector (1 downto 0) ;
9       digit: out std_logic_vector (3 downto 0));
10 end decoder;
11 -----
12 architecture archi_decoder of decoder is
13
14 begin
15     with aff select
16         digit <= "1110" when "00",
17                 "1101" when "01",
18                 "1011" when "10",
19                 "0111" when "11",
20                 "1111" when others;
21
22 end archi_decoder;
23 -----

```

Entity 'Decoder'

The entity 'bcdTo7seg' part has 'di' as the input which is a 'std_logic_vector' of 4 bits and segments as the output which is a 'std_logic_vector' of 7 bits. The architecture 'arCbcdTo7seg' part decides the numbers (0 to 9) based on the input 'di'

```
24  -----
25  library IEEE;
26  use IEEE.STD_LOGIC_1164.ALL;
27  use ieee.std_logic_arith.all;
28  use ieee.std_logic_unsigned.all;
29  -----
30  entity bcdTo7seg is port
31  (di: in std_logic_vector (3 downto 0) ;
32   segments: out std_logic_vector (6 downto 0));
33  end bcdTo7seg;
34  -----
35  architecture arCbcdTo7seg of bcdTo7seg is
36
37  begin
38      with di select
39          segments <= "0000001" when "0000",
40                      "1001111" when "0001",
41                      "0010010" when "0010",
42                      "0000110" when "0011",
43                      "1001100" when "0100",
44                      "0100100" when "0101",
45                      "0100000" when "0110",
46                      "0001111" when "0111",
47                      "0000000" when "1000",
48                      "0000100" when "1001",
49                      "1111111" when others;
50
51  end arCbcdTo7seg;
52  -----
```

Entity 'BcdTo7seg'

- The entity 'counter' has 'clk' as input of type 'std_logic' which is used for the counter to start counting at every rising edge of the clock.
- 'di' as output of type 'std_logic_vector' of 4 bits which is used for selecting the number to be displayed from 0 to 9 in the 7-segment display.

- 'aff' as output of type '*std_logic_vector*' of 2 bits which is used for selecting the digit place to display the number

```

53  -----
54  library IEEE;
55  use IEEE.STD_LOGIC_1164.ALL;
56  use ieee.std_logic_arith.all;
57  use ieee.std_logic_unsigned.all;
58  -----
59  entity counter is port
60      (clk: in std_logic;
61       di: out std_logic_vector (3 downto 0);
62       aff: out std_logic_vector (1 downto 0)) ;
63  end counter;
64  -----
65  architecture archi_counter of counter is
66
67      signal count: integer :=0 ;
68      signal divclk: std_logic :='0';
69      signal affc:std_logic_vector (1 downto 0);
70

```

Entity '*Counter*'

In the architecture we made two processes. First process is used for division of the clock frequency from 8 Mhz to a lower value. This done by using a signal count which is incremented every rising edge of the clock and once the value of the count reaches 400000 then the new clock is generated and this repeats as long as the clock is available.

The second process uses this newly generated clock to initialize the process and, in this process, for every rising edge of the new clock the digits as well as the digit place is selected.

```

70
71     begin
72         process(clk)
73         begin
74             if rising_edge(clk) then
75                 count <= count + 1;
76                 if cn = 4000000 then
77                     divclk <= not(divclk);
78                     count <= 0;
79                 end if;
80             end if;
81         end process;
82
83         process(divclk)
84         begin
85             if rising_edge(divclk) then
86
87                 case affc is
88                     when "00" => di <= "1000";
89                     when "01" => di <= "0001";
90                     when "10" => di <= "0000";
91                     when "11" => di <= "0010";
92                     when others => di <= "0000";
93                 end case;
94                 affc<=affc+1;
95                 aff<=affc;
96             end if;
97         end process;
98
99     end archi_counter;

```

The entity 'pro4' part has 'digit' as the output with 'std_logic_vector' of 4-bits' which is used to select the digit place and 'segments' as the output with 'std_logic_vector' of 7-bits which displays the digit and 'clk' as input of type 'std_logic' which is used for the counter to start counting at every rising edge of the clock.

The architecture 'archi_prog4' part uses the signal 'aff' and 'di'. Now we use the decoder and 7-segment display and counter written before as components in this program. The components 'decoder', 'bcdTo7seg' and 'Counter' are defined in the architecture 'archi_prog4' part before the program begins.

```

100 -----
101 -----
102 entity prog4 is port
103     ( digit: out std_logic_vector (3 downto 0);
104       segments: out std_logic_vector (6 downto 0);
105       clk: in std_logic;
106       bp0,bp1: in std_logic);
107 end prog4;
108 -----
109 architecture archi_prog4 of prog4 is
110
111     signal aff: std_logic_vector (1 downto 0) ;
112     signal di: std_logic_vector (3 downto 0) ;
113
114     component decoder port
115         (aff: in std_logic_vector (1 downto 0) ;
116          digit: out std_logic_vector (3 downto 0));
117     end component;
118
119     component bcdTo7seg port
120         (di: in std_logic_vector (3 downto 0) ;
121          segments: out std_logic_vector (6 downto 0));
122     end component;
123
124     component counter port
125         (clk: in std_logic;
126          di: out std_logic_vector (3 downto 0);
127          aff: out std_logic_vector (1 downto 0) := "00");
128     end component;
129 -----
130

```

Now we use a command named "portmap" and using this 'aff' and 'digit' are port mapped, 'di' and 'segments' are port mapped and 'aff', 'clk' and 'di' are port mapped. Now the output of the display is "2008"

```

129 -----
130 -----
131 begin
132
133     digit: decoder
134         port map ( aff, digit);
135     segment: bcdTo7seg
136         port map (di, segments);
137     counter: counter
138         port map (clk, di, aff );
139
140 end archi_prog4;
141 -----
142 -----

```

 


Fig 4: Results obtained

Question 4: To implement a calculator using Xilinx cool runner II

The goal of this lab is to implement a calculator in Xilinx cool runner with the following requirements:

$z = x \sim y$ with


- \sim operator is either + or - or *
- x on the left digit (Digit 3)
- y on Digit 2
- z on the 2 right digits (Digit 1 Digit 0)

Choose x and y:

- x increments (modulo 10) each time you press BP0
- y increments (modulo 10) each time you press BP1

Operator is fixed by switch SW0 and SW1:

- + if SW0 = 0 and SW1 = 0
- - if SW0 = 1 and SW1 = 0
- * if SW1 = 1

 

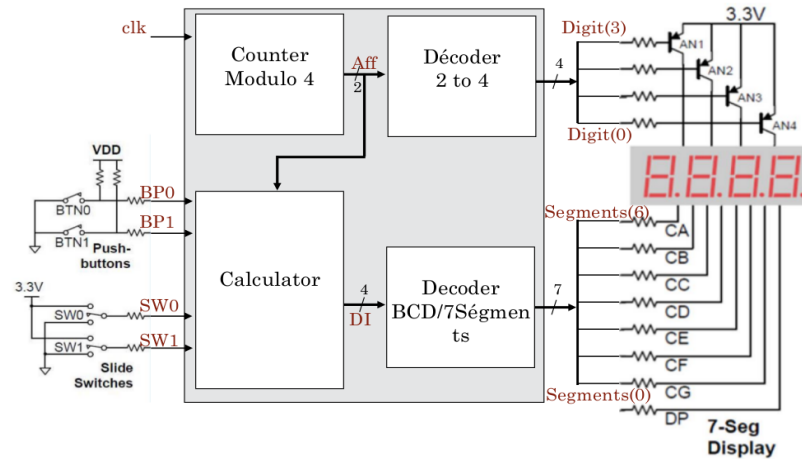


Fig 5: Circuit for the calculator

This program was done using 5 entities and they are:

- 'Decoder' for selecting the digit place to be displayed.
- 'BcdTo7seg' to display the digit in the 7-segment display.
- 'Counter' to do a modulo 4 counter operation.
- 'Calculator' to do the operation on the inputs and also to input the numbers and operands
- 'Program5' to combine all these entity as components and then display the output on the 7-segment display as per the specifications

Entity 'Decoder'

The entity decoder has 'aff' as input of type 'std_logic_vector' of 2-bits and 'digit' as output of type 'std_logic_vector' of 4-bits. The architecture part of the decoder decides the behavior of the decoder. The 'aff' is used to select a particular 'digit' in the display.

```

1
2
3  library IEEE;
4  use IEEE.STD_LOGIC_1164.ALL;
5  use ieee.std_logic_arith.all;
6  use ieee.std_logic_unsigned.all;
7
8
9  entity decoder is port
10 (aff: in std_logic_vector (1 downto 0) ;
11  digit: out std_logic_vector (3 downto 0));
12 end decoder;
13
14 architecture archi_decoder of decoder is
15
16 begin
17     with aff select
18         digit <= "1110" when "00",
19                 "1101" when "01",
20                 "1011" when "10",
21                 "0111" when "11",
22                 "1111" when others;
23
24 end archi_decoder;
25

```

Entity *BcdTo7seg*'

The entity 'bcdTo7seg' part has 'di' as the input which is a 'std_logic_vector' of 4 bits and segments as the output which is a 'std_logic_vector' of 7 bits. The architecture 'arCbdToseg' part decides the numbers (0 to 9) based on the input 'di'

```
25 -----
26 library IEEE;
27 use IEEE.STD_LOGIC_1164.ALL;
28 use ieee.std_logic_arith.all;
29 use ieee.std_logic_unsigned.all;
30
31 entity bcdTo7seg is port
32 (di: in std_logic_vector (3 downto 0) ;
33  segments: out std_logic_vector (6 downto 0));
34 end bcdTo7seg;
35
36 architecture archi_7seg of bcdTo7seg is
37
38 begin
39     with di select
40         segments <= "0000001" when "0000",
41                    "1001111" when "0001",
42                    "0010010" when "0010",
43                    "0000110" when "0011",
44                    "1001100" when "0100",
45                    "0100100" when "0101",
46                    "0100000" when "0110",
47                    "0001111" when "0111",
48                    "0000000" when "1000",
49                    "0000100" when "1001",
50                    "1111111" when others;
51
52 end archi_7seg;
53 -----
```

Entity '*Counter*'

|

The entity 'counter' has 'clk' as input of type 'std_logic' which is used for the counter to start counting at every rising edge of the clock.

'di' as output of type 'std_logic_vector' of 4 bits which is used for selecting the number to be displayed from 0 to 9 in the 7-segment display.

'aff' as output of type 'std_logic_vector' of 2 bits which is used for selecting the digit place to display the number

```

53  -----
54  library IEEE;
55  use IEEE.STD_LOGIC_1164.ALL;
56  use ieee.std_logic_arith.all;
57  use ieee.std_logic_unsigned.all;
58
59  entity counter is port
60  (clk: in std_logic;
61  aff: out std_logic_vector (1 downto 0)) ;
62  end counter;
63
64  architecture archi_counter of counter is
65  signal cn: integer :=0 ;
66  signal divclk: std_logic :='0';
67  signal affc:std_logic_vector (1 downto 0);
68  begin
69
70  Clock_div: process(clk)
71  begin
72      if clk'event and clk='1' then
73          cn <= cn + 1;
74          if cn= 400000 then
75              divclk <= not(divclk);
76              cn<=0;
77          end if;
78      end if;
79  end process;
80  pfs1: process(divclk)
81  begin
82      if divclk'event and divclk='1' then
83
84          affc<=affc-1;
85          aff<=affc;
86      end if;
87  end process;
88
89  end archi_counter;
90  -----

```

Entity 'Calculator'

The entity takes 'bp0', 'bp1', 'sw0', 'sw1' as inputs of 'std_logic' in order to get inputs from the switches, 'aff' as input of 2-bits of type 'std_logic_vector' and 'di' of 4-bits as output of type 'std_logic_vector'.

In the architecture of the calculator we need 5 signals of type 'std_logic_vector' and 4-bits each. This is for performing the operations as well as selecting the units and tens place in the display.

```

90  -----
91  library IEEE;
92  use IEEE.STD_LOGIC_1164.ALL;
93  use ieee.std_logic_arith.all;
94  use ieee.std_logic_unsigned.all;
95
96  entity calculator is port
97  (
98  bp0,bp1 : in std_logic;
99  sw0,sw1 : in std_logic;
100  aff: in std_logic_vector(1 downto 0);
101  di: out std_logic_vector(3 downto 0));
102  end calculator;
103
104  architecture archi_calculator of calculator is
105  signal x: std_logic_vector (3 downto 0)
106  signal y: std_logic_vector (3 downto 0)
107  signal z: std_logic_vector (7 downto 0)
108
109  signal units: std_logic_vector (3 downto 0)
110  signal tens: std_logic_vector (3 downto 0)
111
112  -----

```

The process '*increment_XY*' is used for incrementing the values of '*x*' and '*y*' and this process is triggered using the outputs of the button switches '*bp0*', '*bp1*'. Modulo 10 operation is done because we want only the numbers from 0 to 9.

- *x* increments (modulo 10) each time you press BP0
- *y* increments (modulo 10) each time you press BP1

The process '*operation*' is used for selecting the operands. The process is triggered when it receives signal from '*sw0*', '*sw1*'.

- + if SW0 = 0 and SW1 = 0
- - if SW0 = 1 and SW1 = 0
- * if SW1 = 1

```

112 -----
113 begin
114 increment_XY: process(bp0,bp1)
115 begin
116     if bp0'event and bp0 = '0' then
117         y<=y+1;
118
119     end if;
120     if bp1'event and bp1 = '0' then
121         x<=x+1;
122
123     end if;
124
125     if y="1010" then
126         y<="0000";
127     end if;
128     if x="1010" then
129         x<="0000";
130     end if;
131
132 end process;
133
134 operation: process(sw0,sw1)
135 variable N: integer:=1;
136 -----

```

```

136 -----
137 begin
138     if sw1='0' then
139         if sw0='0' then
140             z<= ("000" & x) + ("000" & y);
141
142         elsif sw0='1' then
143             if x>y then
144                 z<= x-y;
145             else
146                 z<= y-x;
147             end if;
148         end if;
149
150     elsif sw1='1' then
151         z <= x*y;
152     end if;
153 -----

```

This part of the code is used to separate the units and the tens place of the output 'z'. We tried using MOD operator but it did not produce the results as expected so we discussed with other groups and came to this solution. This performs the same operation as that of MOD operator.

The output is processed to determine its units and tens place. This is then used to select the corresponding digits in the 7-segment display.

```
153 -----
154     for N in 1 to 9 loop
155         if (10*N) = z then
156             units <= "0000";
157             tens <= conv_std_logic_vector(N,4);
158             exit;
159         elsif (10*N) > z then
160             units <= z - 10*(N-1);
161             tens <= conv_std_logic_vector(N,4)-1;
162             exit;
163         end if;
164     end loop;
165 end process;
166
167 with aff select
168     di<= y when "10",
169     x when "11",
170     units when "00",
171     tens when "01",
172     "1000" when others;
173
174 end archi_calculator;
175 -----
```

The entity 'program5' is the final entity and it has 'clk', 'bp0', 'bp1', 'sw0', 'sw1' as inputs of 'std_logic', 'digit' as output of 4-bits of type 'std_logic_vector' to select the digits place and 'segments' of 7-bits as output of type 'std_logic_vector' for displaying the numbers on 7-segment display.

In the architecture of program5 we used the concepts of components to make the programming easier. We used the entities 'deoder', 'bcdTo7Seg', 'counter', 'calculator' inside the architecture and now we just need to portmap the inputs and outputs.


```

176  library IEEE;
177  use IEEE.STD_LOGIC_1164.ALL;
178  use ieee.std_logic_arith.all;
179  use ieee.std_logic_unsigned.all;
180
181  entity program5 is port
182  (
183    digit: out std_logic_vector (3 downto 0);
184    segments: out std_logic_vector (6 downto 0);
185    clk: in std_logic;
186    bp0,bp1: in std_logic;
187    sw0,sw1: in std_logic);
188  end program5;
189
190  architecture Behavioral of program5 is
191
192    signal aff: std_logic_vector (1 downto 0) ;
193    signal di: std_logic_vector (3 downto 0) ;
194
195    component decoder port
196      (aff: in std_logic_vector (1 downto 0) ;
197       digit: out std_logic_vector (3 downto 0));
198    end component;
199
200    component bcdTo7seg port
201      (di: in std_logic_vector (3 downto 0) ;
202       segments: out std_logic_vector (6 downto 0));
203    end component;
204
205    component counter port
206      (clk: in std_logic;
207       aff: out std_logic_vector (1 downto 0));
208    end component;
209
210    component calculator port
211      (bp0,bp1 : in std_logic;
212       sw0,sw1 : in std_logic;
213       aff: in std_logic_vector(1 downto 0);
214       di: out std_logic_vector(3 downto 0));
215    end component;

```

- portmap the input 'aff' and output 'digit' of the counter
- portmap the input 'clk' and output 'aff' of the decoder.
- portmap the input 'di' and output 'segments' of the decoder.
- portmap the inputs 'bp0', 'bp1', 'sw0', 'sw1' and outputs 'aff' and 'di' of the decoder.

```

216
217     begin
218     decoder
219         port map ( aff,digit);
220     bcdTo7seg
221         port map (di,segments);
222     counter
223         port map(clk,aff);
224     calculator
225         port map(bp0,bp1,sw0,sw1,aff,di);
226
227     end Behavioral;
228

```

Results obtained

 


Fig 6: Addition operation

 


Fig 7: Multiplication operation

 


Fig 8: Subtraction operation

Video link: <https://drive.google.com/open?id=1c7B8S07kvOYUtDbuzeuENgBPgMNBj9Am>